

# UART Protocol Establishment for Serial Communication(Report-III)

## Udit Jain , Shashwat Shivam

---

### Specifications

We want to design a module on FPGA which will transmit an ASCII characters from board to PC at an agreed frequency say 9600 Baud rate.

This will happen by an agreed upon protocol between them.

### Overall Approach


To transmit an ASCII character we would need 8 bits at a time. To establish a protocol we would need some bit to know that the incoming of the character bits has started so this bit will be called a START BIT . Similarly we would need a STOP BIT to indicate an end of transmission and that Bit will be also be sent when there is no signal to be transmitted . Choices of start and stop can be 0 1 or 1 0 but , we'll go with the industry protocol standard of Start $\leq$ 0 and Stop $\leq$ 1 and there will be a stream of 1's when nothing is being sent, upon encountering the first 0 PC will start listening . The choice of whether to send start as 0 or 1 and to send MSB or LSB first will be dictated also by the protocol to receive programmed in the receiving end of PC.

### Block Diagram

Transmitter has another counter of 10 bits which will select the bit that will be sent from the sequence (start + 8 bits + stop) and transmits the configuration of switches to cable. The display unit will display the

---

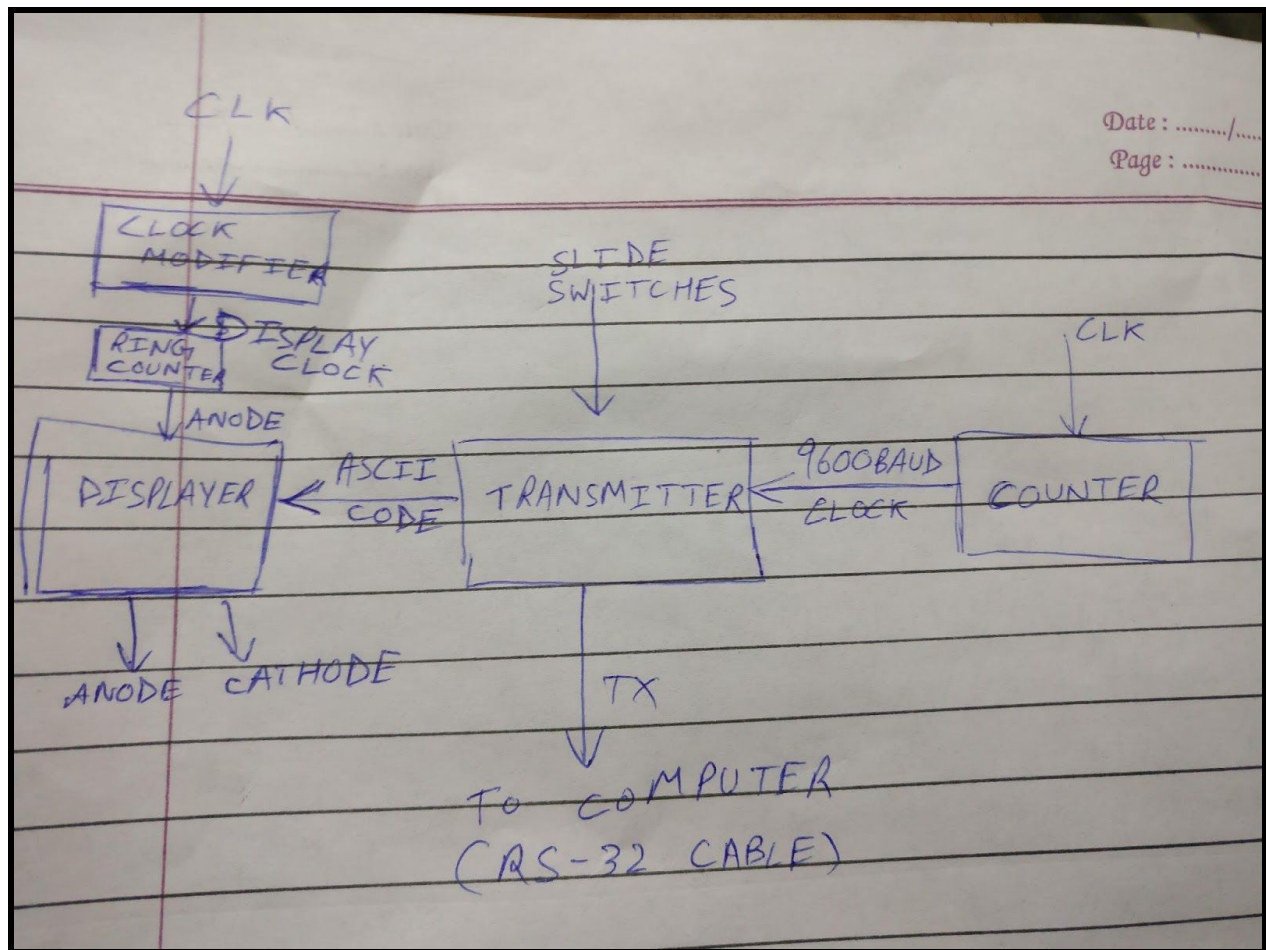current value for the configuration of switches. To transmit the input, we'll hit push button and send .



## Test and Demonstration

We can do loopback testing of the wire . We will take input from the switches on FPGA , display the corresponding ASCII value on the Seven Segment Display and send the same value to PC's receiving terminal.

## Input / Output

Input from switches (16 bits) will be encoded into start bit '0' then two packets of 8 bits each followed by stop bit '1'


A push button will function as send button (which will send the configuration of switches on being pressed)

There will be a push button functioning as reset button

Switch configuration will be shown on LED's and optionally ASCII code will be shown on the SSD.

Output will be on terminal of PC , the two corresponding characters.


## BLOCK DIAGRAM

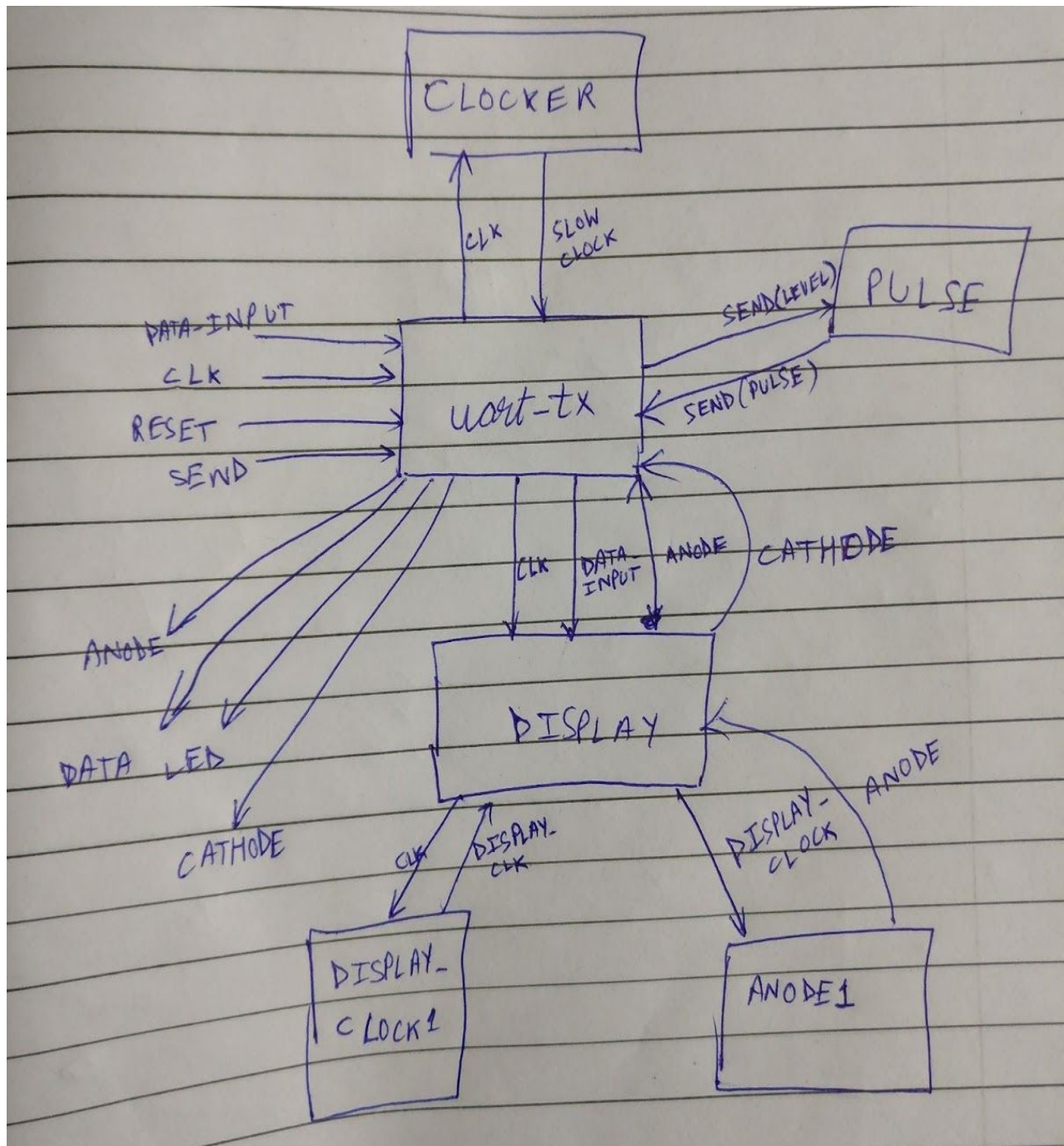


## SERIAL PACKET




## SERIAL TRANSMISSION

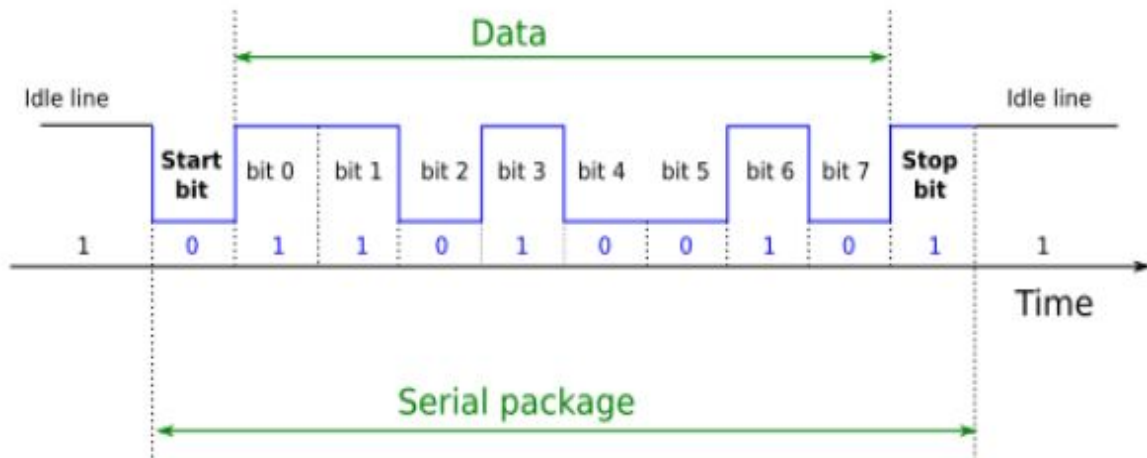


## CHRONOGRAM

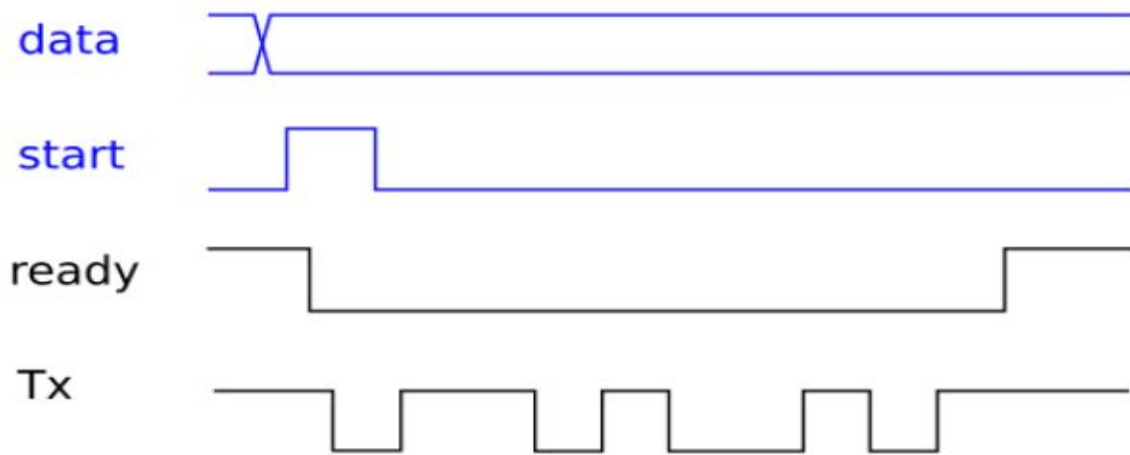

## CONTROLLER FSM

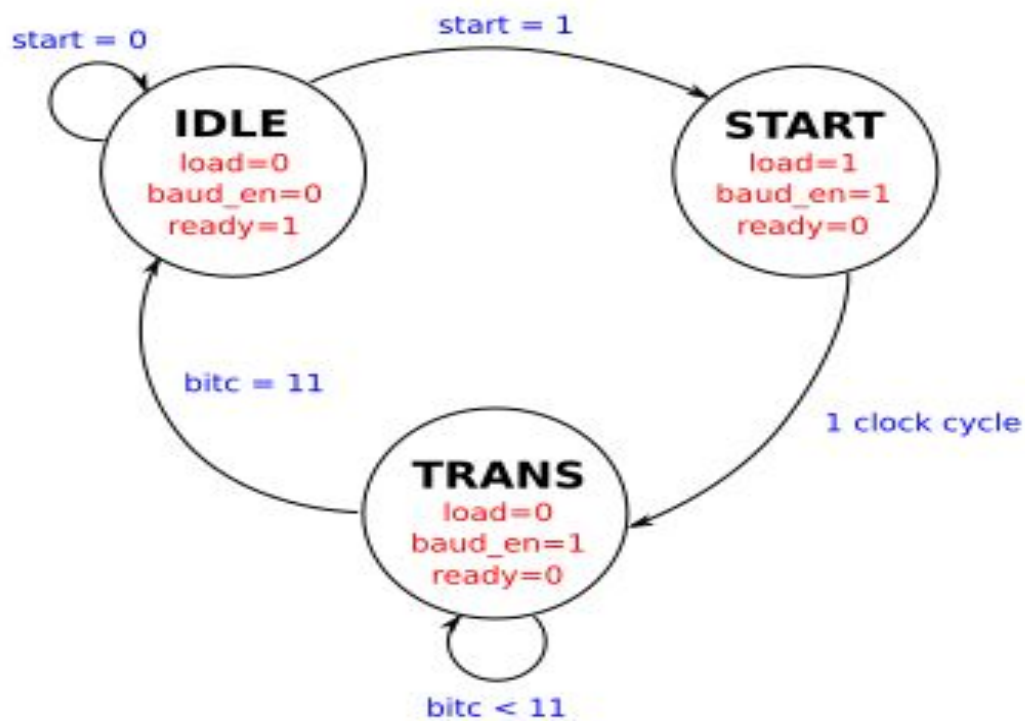

## UART MODULE

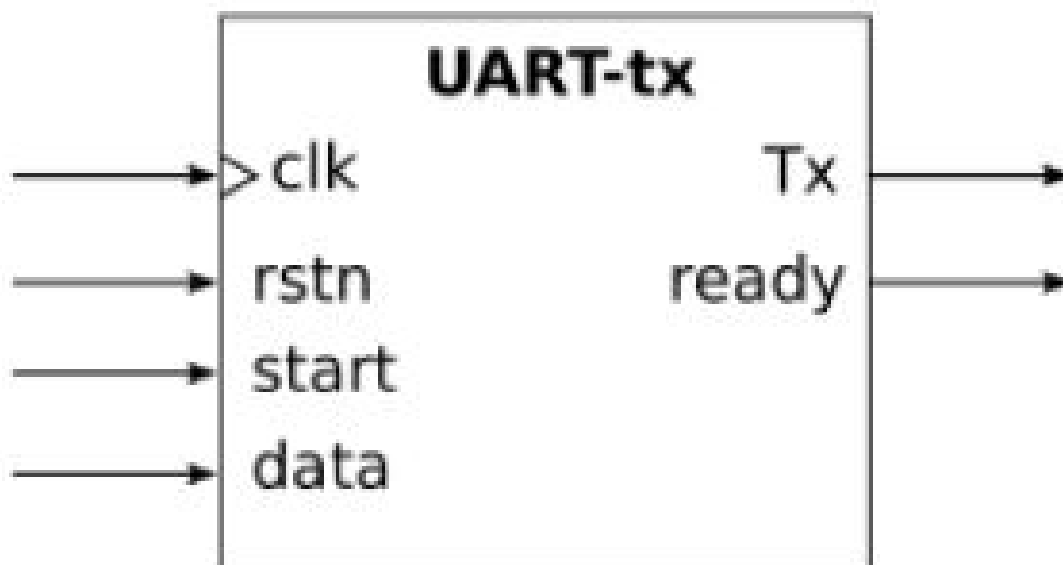



## PSEUDO-CODE

Our code is working excellently in the simulation mode , but we couldn't test it on the board due to some permissions restrictions on listening on the ports on the DHD lab computers. Otherwise the bitstream generated just fine.

```
when( send='1' & !busy)
    send start-bit , busy<='1'
    increment counter
else if( counter != "000000000")
    send bit at the position where
    counter has bit 1
    counter <= shift-left(counter)
else if( counter = "100000000")
    send stop-bit
    busy<='0'
    counter <= "000000000"
```


DO THIS on rising edge of 9600 Hz clock.


## TESTING & SIMULATION

```
cs1160327@beas2:~$ cat /dev/tty
tty      tty21      tty35      tty49      tty62      ttyS17      ttyS30
tty0      tty22      tty36      tty5      tty63      ttyS18      ttyS31
tty1      tty23      tty37      tty50      tty7      ttyS19      ttyS4
tty10     tty24      tty38      tty51      tty8      ttyS2      ttyS5
tty11     tty25      tty39      tty52      tty9      ttyS20      ttyS6
tty12     tty26      tty4      tty53      ttyprintk  ttyS21      ttyS7
tty13     tty27      tty40      tty54      ttyS0      ttyS22      ttyS8
tty14     tty28      tty41      tty55      ttyS1      ttyS23      ttyS9
tty15     tty29      tty42      tty56      ttyS10     ttyS24      ttyUSB1
tty16     tty3      tty43      tty57      ttyS11     ttyS25
tty17     tty30      tty44      tty58      ttyS12     ttyS26
tty18     tty31      tty45      tty59      ttyS13     ttyS27
tty19     tty32      tty46      tty6      ttyS14     ttyS28
tty2      tty33      tty47      tty60      ttyS15     ttyS29
tty20     tty34      tty48      tty61      ttyS16     ttyS3

cs1160327@beas2:~$ cat /dev/ttyUSB1
```

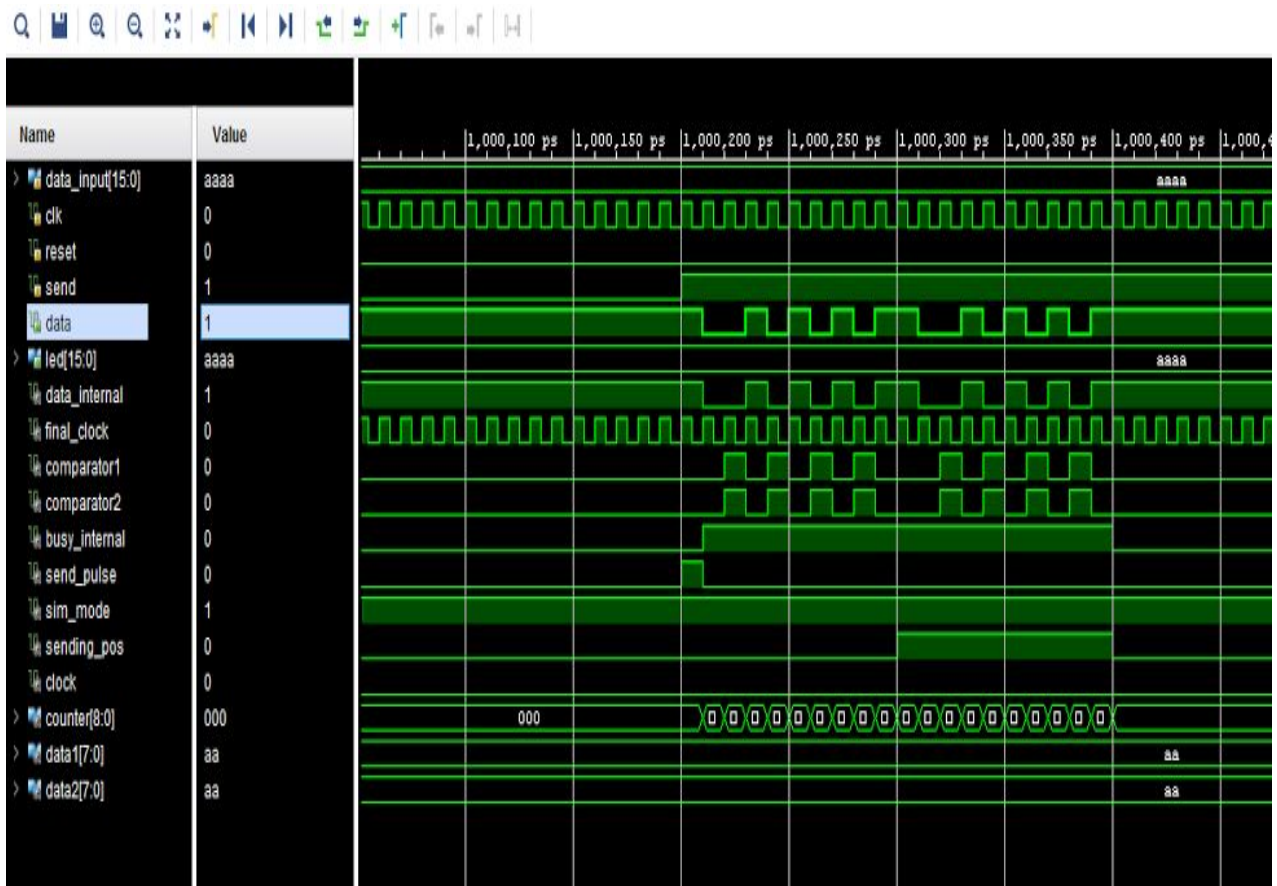
This cat/dev/ttyUSB1(from FPGA) will enable us to listen on that port , given if it's permissible. Other tty's are the other ports we can listen on.



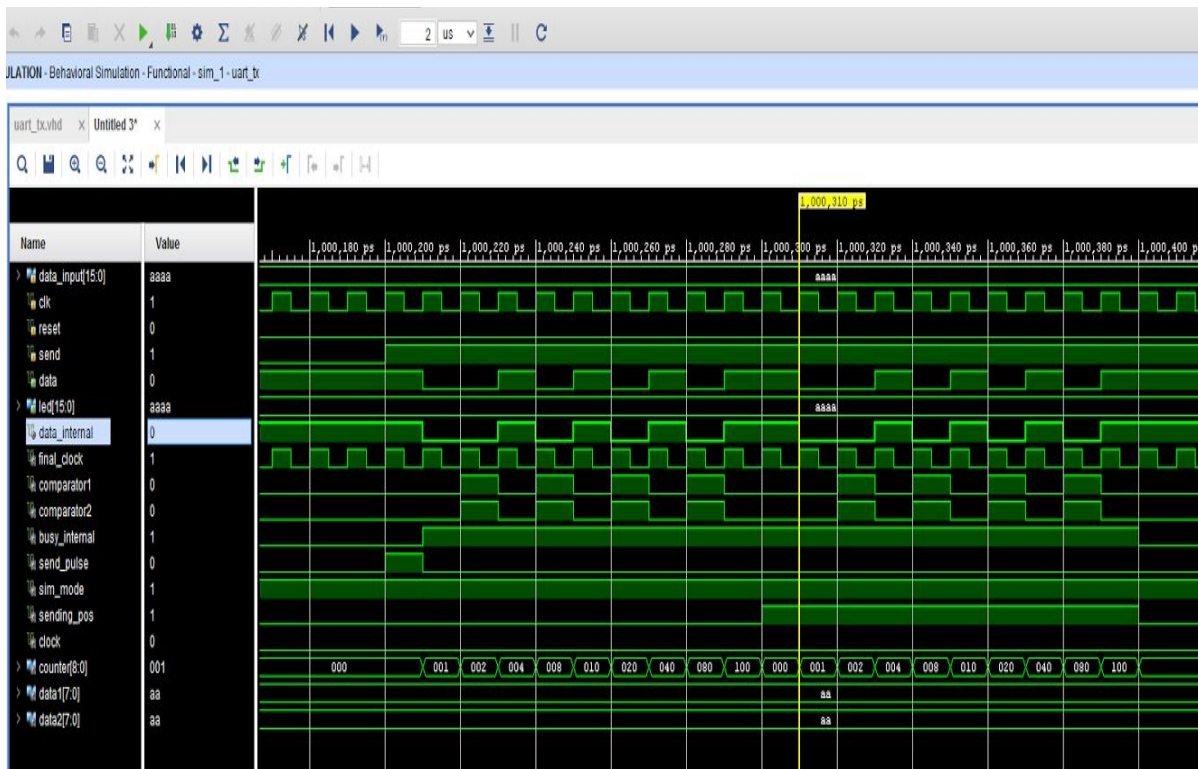
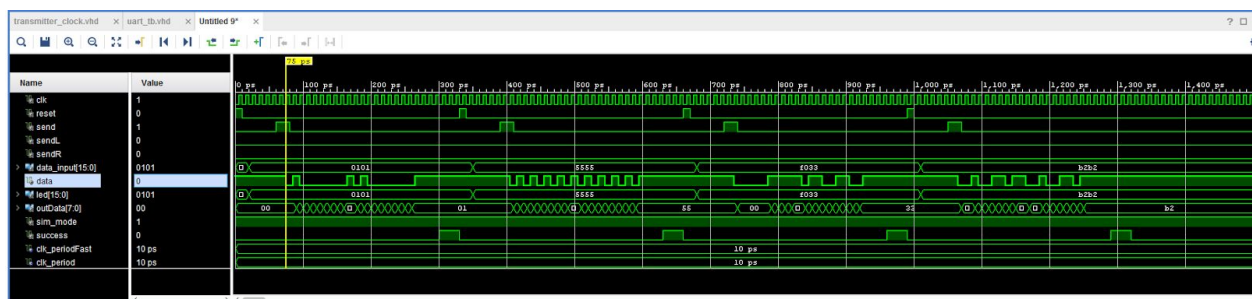
## TESTBENCH TESTING OF MAIN MODULE

The main module was tested using a testbench run in simulation. The simulation was designed to send a clock pulse for 3-4 clock cycles. After sending a pulse start bit (= '0') was tested and consequently the bits of the sent data (data signal was set prior to the test case and then wait was applied for a few clock cycles) was checked in data signal in each cycle and also in the reverse order i.e. the LSB ( Least Significant Bit ) first to the MSB ( Most Significant Bit). After this the data was checked for stop bit (= '1'). After this the signal was tested to give '1' signal if sent is not 1 and no data is being sent. Many random combinations of bits was checked for consistency. The test bench file has been attached along with the report. A few images of the testing are as shown below :-







```
Tcl Console x Messages Log
# }
# run 1000ns
Note: Test Case 1 succesfully cleared
Time: 300 ps Iteration: 0 Process: /uart_tb/stim_proc File: C:/Users/Shashwat Shivam/Desktop/Project215/uart_tb.vhd
Note: Test Case 2 succesfully cleared
Time: 630 ps Iteration: 0 Process: /uart_tb/stim_proc File: C:/Users/Shashwat Shivam/Desktop/Project215/uart_tb.vhd
Note: Test Case 3 succesfully cleared
Time: 960 ps Iteration: 0 Process: /uart_tb/stim_proc File: C:/Users/Shashwat Shivam/Desktop/Project215/uart_tb.vhd
Note: Test Case 4 succesfully cleared
Time: 1290 ps Iteration: 0 Process: /uart_tb/stim_proc File: C:/Users/Shashwat Shivam/Desktop/Project215/uart_tb.vhd
Note: Testbench of UART completed successfully!
Time: 1320 ps Iteration: 0 Process: /uart_tb/stim_proc File: C:/Users/Shashwat Shivam/Desktop/Project215/uart_tb.vhd
Note: TEST BENCH MADE BY: UDIT JAIN (2016CS10327) , SHASHWAT SHIVAM (2016CS10328)
Time: 1320 ps Iteration: 0 Process: /uart_tb/stim_proc File: C:/Users/Shashwat Shivam/Desktop/Project215/uart_tb.vhd
INFO: [USF-XSim-96] XSim completed. Design snapshot 'uart_tb_behav' loaded.
INFO: [USF-XSim-97] XSim simulation ran for 1000ns
launch_simulation: Time (s): cpu = 00:00:03 ; elapsed = 00:00:06 . Memory (MB): peak = 1666.445 ; gain = 0.000
run 1400 ps
```
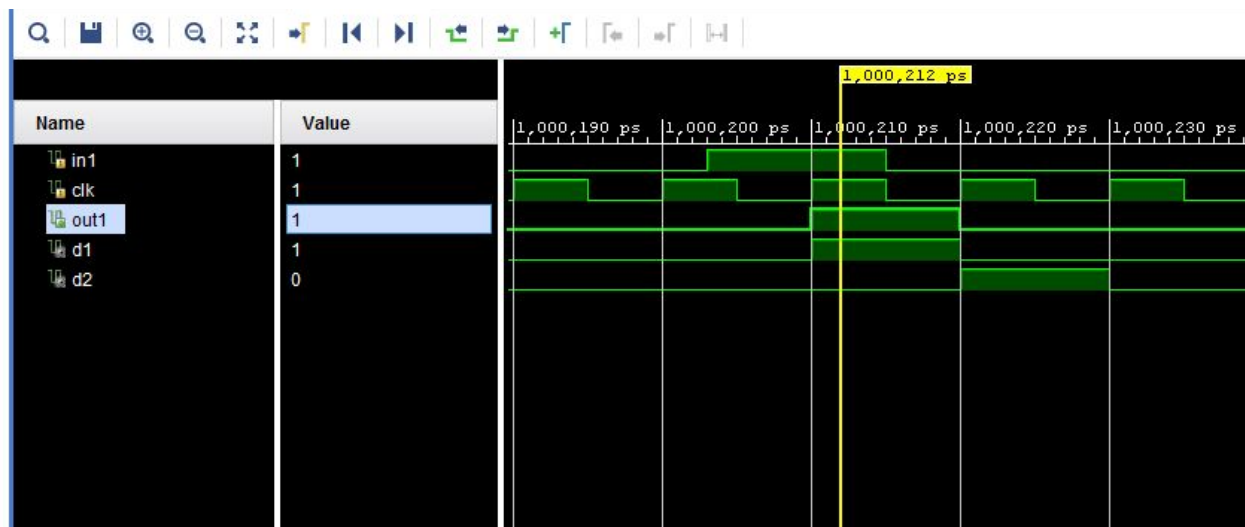
## UNIT TESTING USING SIMULATION


The subunits were tested separately using simulation. The images are as follows :-



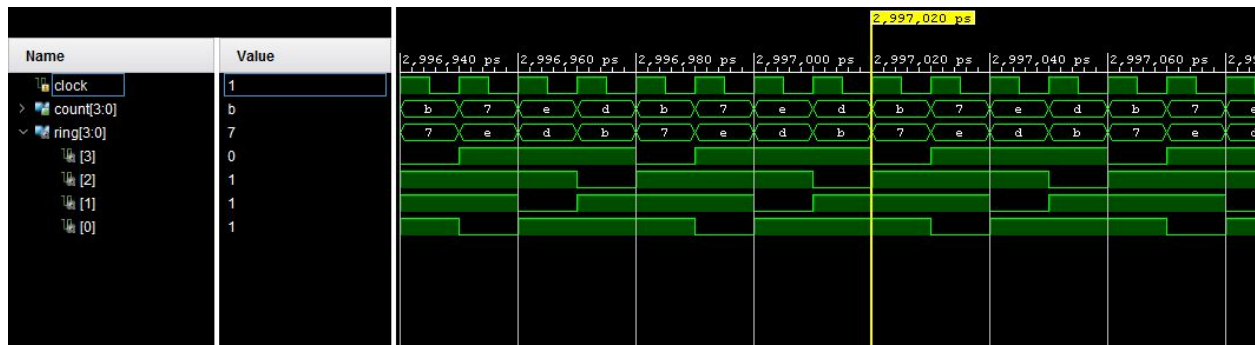
The above waveform is for the **level to pulse converter**. 'In1' is the level input signal which is converted to 'out1' pulse.



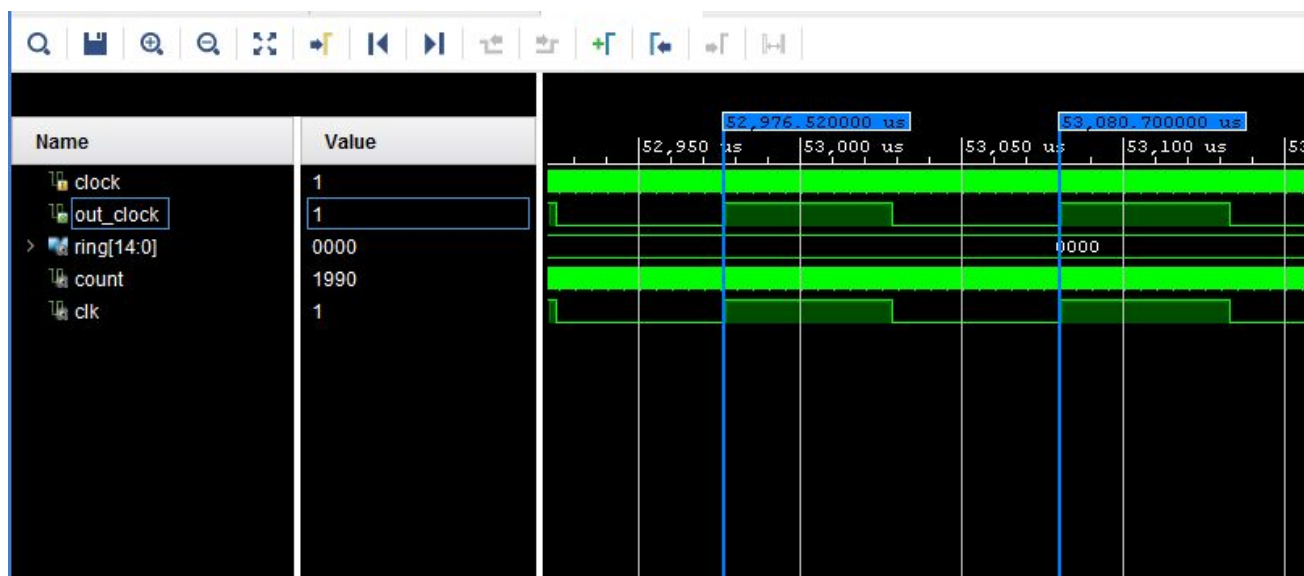The above waveform is for the **ring counter**. The display clock (clock modified to use on seven segment display) is the input. The output are the corresponding anode values which shift the 0 to left circularly on every clock cycle. The outputs are of the form :- '1110' -> '1101' -> '1011' and so on.



The above waveform is of the **transmission clock modifier**. On running the simulation clock at 100MHz ( time period 10ns) we get a modified clock with time period (53080.70 us - 52976.52 us = ) 104.18 us which is almost equal 9600 Hz ( 9598.77 Hz). This modified clock will thus help us to send a data signal at 9600 bits per second ( 9600 bauds). It works using a counter to count circularly upto 5208 on every clock edge.

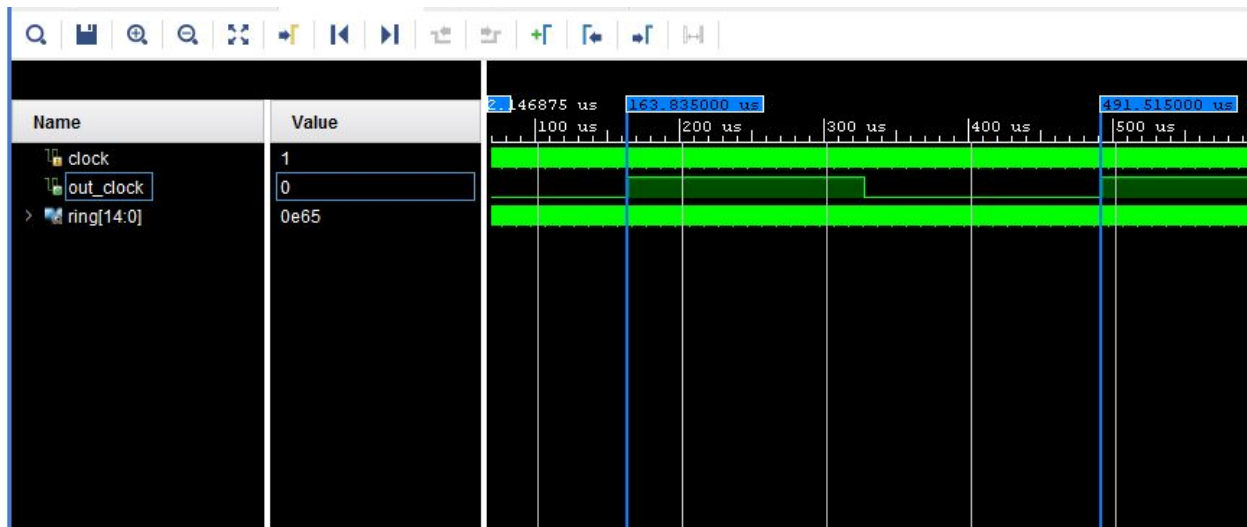

The above waveform is of the **display clock modifier** ( for SSD clock). Its design is similar to the transmission clock modifier and suitable output is created similarly.


### TESTING ON BOARD

The code was uploaded onto an FPGA and tested using Putty and debugged. The errors encountered on doing so were:-

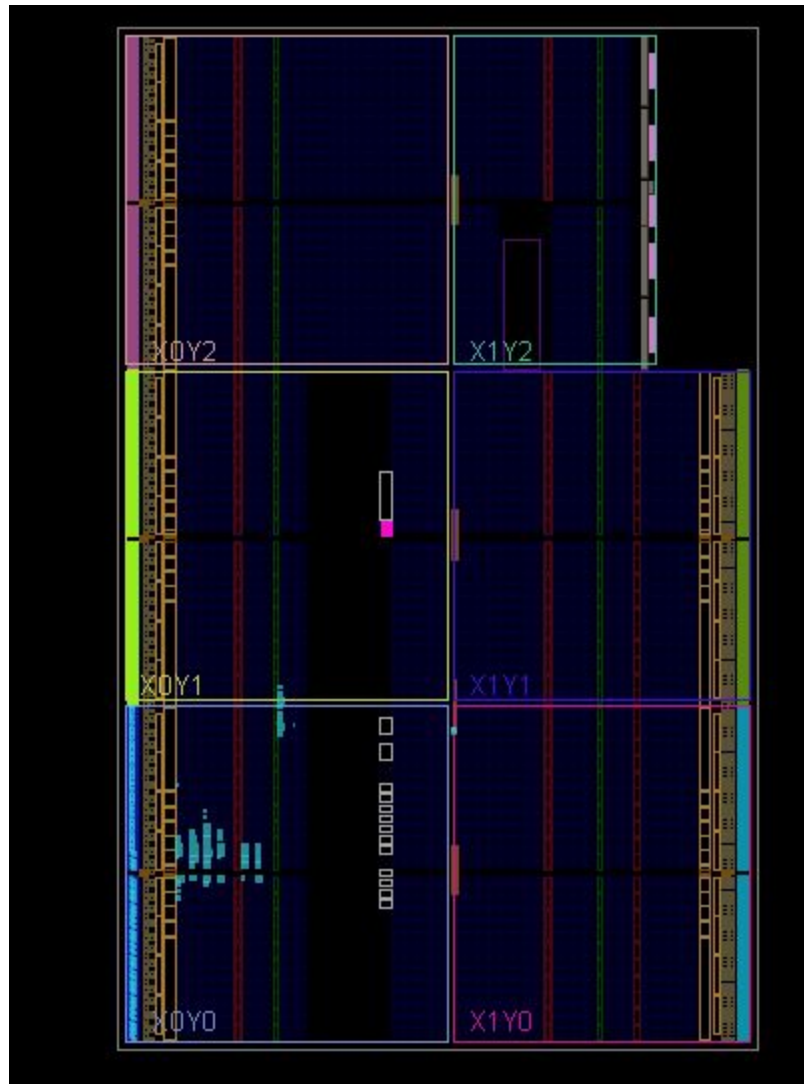1. Initially no output was visible. No transmission light was also blinking on the FPGA. The reason of this error was found that the pulse of the send button signal was too short to be caught within a clock cycle. This was then corrected.
2. Next we encountered error relating to garbage output on the terminal. On observing the ascii values of the characters output on the terminal it was found that the baud rate was not in sync. The baud rate being half of 9600 each bit was being received twice by the computer terminal. This was then corrected by changing the counter value in the transmission clock modifier entity. After this the output was as expected.

The images of the output on Putty will be put up in next report.

The image of the implemented design is as follows:-




## MODIFICATIONS AND EXTRA FEATURES

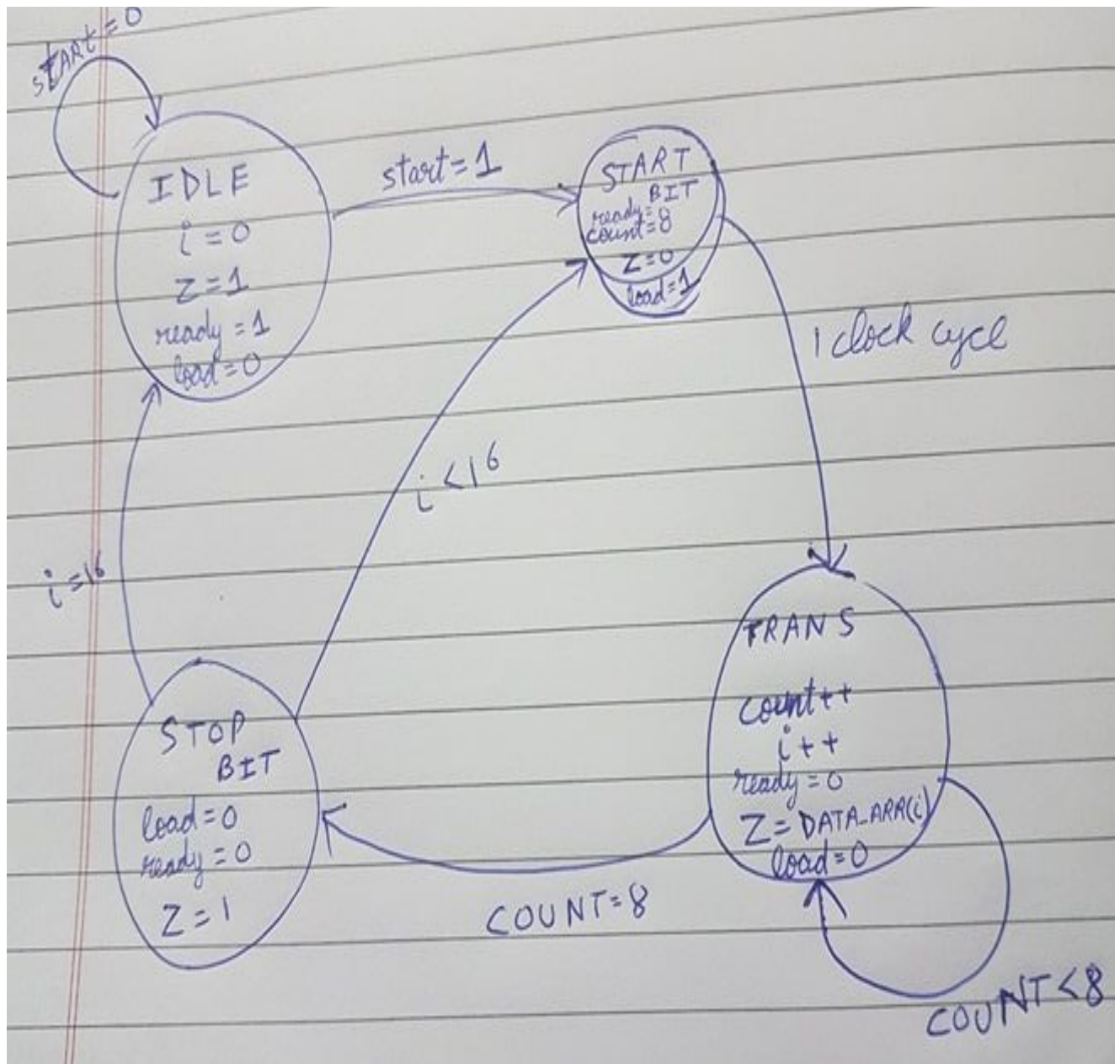
1. The 16 switches were used to send bits as pairs ( two 8 bit ASCII codes.)
2. The extra buttons on the FPGA were used to program saved messages or images to be displayed on pressing them.
3. The SSD will be used to display the ASCII code that has been set on the switches to aid the user in setting ASCII codes faster.



The modified state diagram for sending 2 ASCII codes back to back is as follows:-



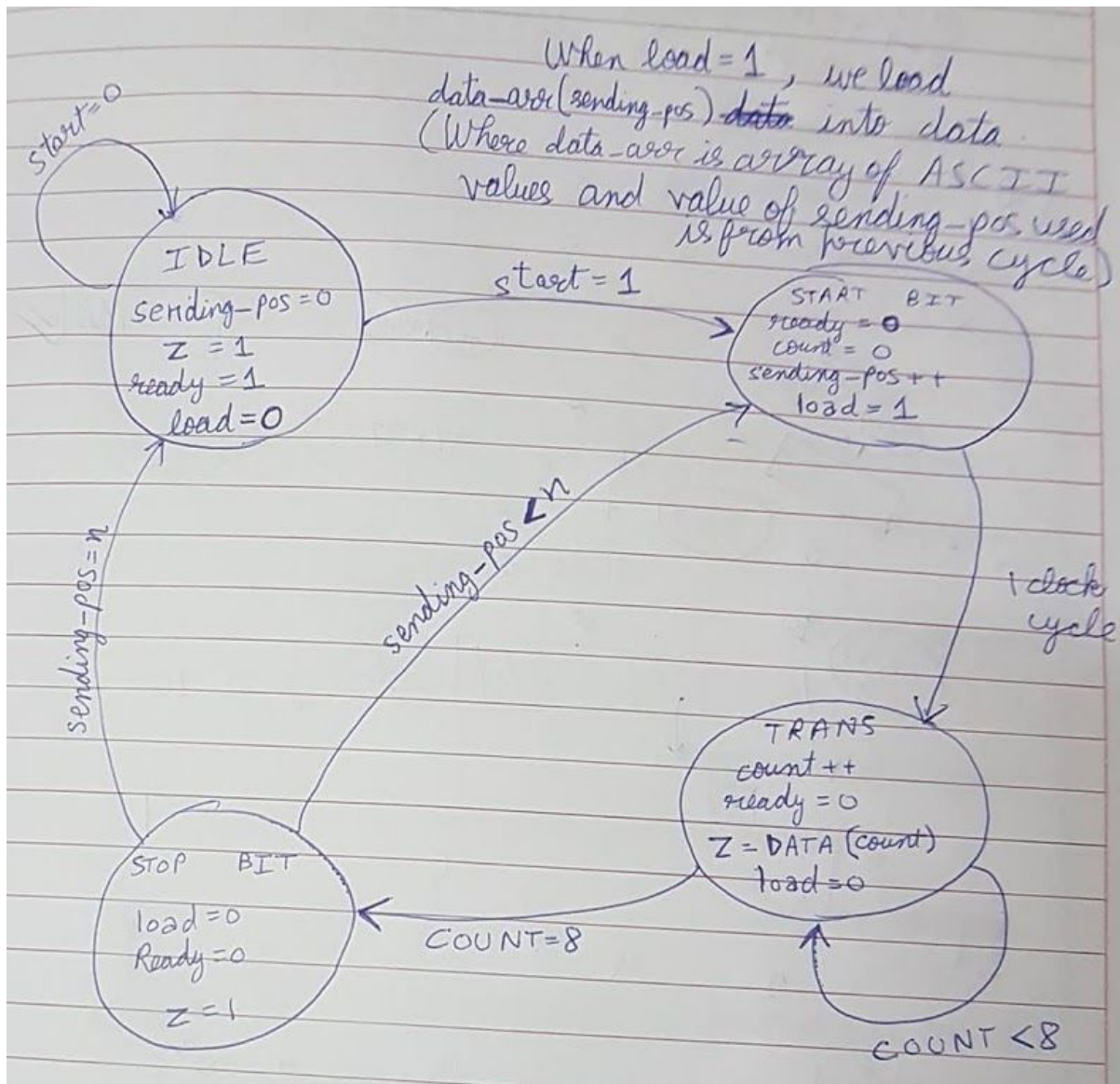This state diagram is then generalized to send 'n' ASCII values to send pre-saved long messages. The image is as follows:-



Udit Jain - 2016CS10327

Shashwat Shivam - 2016CS10328